

ModSim Project 2: Optimal Configuration of a Second Order High Pass Filter


Shreya Chowdhary and Kyle McCracken

What is the configuration of resistors and capacitors in a second order high pass filter that would result in a bode plot that aligns perfectly (or as close as possible) to the theoretical model for a high pass filter?


The bode plots for second order high pass filters don't exactly match the theoretical model for a second-order high pass filter (while first-order high pass filters do match the theoretical model). This is due to an exchange of current between the two high-pass filters. Thus, we decided to create a model that would determine the optimal combination of resistors and capacitors for a given τ to minimize current flow between the two high pass filters in order to minimize the error between the theoretical bode plot and the simulated bode plot.

Methodology

We consider the following circuit:

 

 In this circuit, we use V_{in} where $V_{in} = A \sin 2\pi ft$ to represent the sinusoidal input waveform, V_m to represent the voltage at the branch between the two high-pass filters, and V_{out} to represent the output voltage. We use our voltages as the stocks for our stock and flow diagram (shown below).



Through circuit analysis, we derived differential equations for the flows:

$$\begin{aligned}\frac{dV_{in}}{dt} &= 2\pi A f \cos 2\pi f t \\ \frac{dV_m}{dt} &= \frac{dV_{in}}{dt} - \frac{\frac{V_m}{R_1} + \frac{V_{out}}{R_2}}{C_1} \\ \frac{dV_{out}}{dt} &= \frac{dV_m}{dt} - \frac{V_{out}}{R_2 C_2}\end{aligned}$$

The only assumption we made was a certain amount of instantaneousness in the change of voltage, which is a valid assumption based on our knowledge of how voltage responds to current.

```

In [ ]: # Configure Jupyter so figures appear in the notebook
        %matplotlib inline

        # Configure Jupyter to display the assigned value after an assignment
        %config InteractiveShell.ast_node_interactivity='last_expr_or_assign'

        from modsim import *

        # Creating the initial state
        init = State(Vm=0,
                     Vout=0)

        # Initializing the configuration of the high pass filter
        params = Params(R1=1000000,
                        R2=1000000,
                        C1=1e-11,
                        C2=1e-11)

        # Initializing the system configurations
        # freqs is the number of frequencies to sweep through
        # numwavs is the number of wavelengths simulated per frequency
        # stepres is ...?
        setsystem = System(tau = 1.5e-7,
                           A=0.5, #Amplitude of Vin wave
                           init=init,
                           t0=0,
                           freqs = 8,
                           stepres = 200,
                           numwavs = 4)

        def make_system(params, setsystem):
            '''
            Creates a system object.
            '''
            # param params: the configuration for the circuit (R1, R2)

            # Creates a system object representing the circuit with the correct configuration.
            print('making system')
            R1, R2, C1, C2 = params

            # Sets the configuration of the filter
            setsystem.set(params = params)

            # Determines the characteristic cut off frequency
            fc = 1/(2*np.pi*setsystem.tau)

            # Determines the maximum and minimum for the range of frequencies
            # to sweep when creating the bode plot
            # These frequencies will be 2 orders of magnitude above and
            # below the cut-off frequency
            flow = int(np.log10(fc))-2
            fhigh = int(np.log10(fc))+2

            setsystem.set(f1 = flow, f2 = fhigh)
            print('made system')
            system = setsystem

            return system

        def slope_func(init, t, system):

```

```

'''
Determines the ODEs for Vin, Vm, and Vout, which will be used
later for the ODE solver.
'''

# param init: the initial state of the system
# param t: the time at which this function will be evaluated
# param system: the system object

unpack(system)
R1, R2, C1, C2 = system.params

vm, vout = init

# ODEs for Vin, Vm, Vout
# We treat dVin as a variable because Vin is not influenced by Vm or Vout, but influ
ences both
dvin = 2 * np.pi * A * f * np.cos(2*np.pi*f*t)
dvm = dvin - (vm/R1 + vout/R2) / C1
dvout = dvm - vout / (R2*C2)

return dvm, dvout

def run_bode(system):
'''
Generates a bode plot for the given set of frequencies.
'''
# param system: the system object

unpack(system)
print('start bode')

# Creates a set of frequencies on a log scale
farray = np.logspace(f1, f2, freqs)

Re = TimeSeries()

for f in farray:
    system.set(f=f, t_end = numwavels / f)

    # Determines the maximum step length, to force the bode plot to run faster
    max_step = (system.t_end - t0) / (stepres)
    results, details = run_ode_solver(system, slope_func, max_step = max_step)

    # Uses nfev for the # of steps and to select out the tail
    tail = int(details.nfev/(2*np.pi*numwavels))
    amplitudeM = results.Vout.tail(tail).ptp()
    Re[f] = amplitudeM

print('done bode')
return Re

def run_freq(system):
'''
Runs the simulation for a specific frequency (in this case, the cut off frequency).
'''

print('start freq')

# Calculates the cut off frequency
fc = 1/(2*np.pi * system.tau)
print(fc)

```

```
# Sets the frequency to run the bode plot at to the cut off  
system.set(f = fc)
```

```
system.set(t_end = system.numwavels / system.f)  
unpack(system)
```

```
max_step = (t_end - t0) / (stepres)
```

```
results, details = run_ode_solver(system, slope_func, max_step = max_step)  
tail = int(details.nfev/(2*np.pi*numwavels))  
amplitudeM = results.Vout.tail(tail).ptp()
```

```
print('done freq')  
return amplitudeM
```

```
def run_calc(system):  
    '''
```

```
Determines what the theoretical model should look like for the given frequencies  
    '''
```

```
    unpack(system)  
    farray = np.logspace(f1, f2, freqs)  
    C = TimeSeries()
```

```
    for f in farray:
```

```
        # Uses circuit theory to calculate the amplitude  
        w = 2*np.pi*f  
        rcw1 = tau*w  
        rcw2 = tau*w  
        amplitudeC = (rcw1*rcw2) / (np.sqrt(1 + rcw1**2) * np.sqrt(1 + rcw2**2))  
        C[f] = amplitudeC
```

```
    return C
```

```
def error_func(params, setsystem):  
    '''
```

```
Determines the error between the simulated bode plot and the theoretical bode plot.  
    '''
```

```
    system = make_system(params, setsystem)  
    print(params)  
    print('start error')  
    #ampM = run_freq(system)  
    #ampC = system.A
```

```
    results = run_bode(setsystem)  
    calcs = run_calc(setsystem)
```

```
    errors = results - calcs  
    print('done error')  
    return errors
```

```
def plot_bode_plot():  
    '''
```

```
Plots the simulated bode plot against the theoretical model  
    '''
```

```
    fig = plt.figure()  
    ax = fig.add_subplot(111)  
    ax.set_xscale('log')  
    lns1 = ax.plot(results, label = 'simulated')  
    lns2 = ax.plot(run_calc(system), label = 'calculation')
```

```
lns = lns1+lns2
labs = [l.get_label() for l in lns]
ax.legend(lns, labs, loc = 'best')
savefig('graphs\BodePlotLowRes2.png')

best_params, fit_details = fit_leastsq(error_func, params, setsystem, maxfev = 500)
print(best_params, setsystem.tau/best_params.R1, setsystem.tau/best_params.R2)

system = make_system(best_params, setsystem)
results = run_bode(system)
plot_bode_plot()
```

Results

According to our model, the optimal configuration for resistors and capacitors in a second order high pass filter with a tau of $1.5e-7$ would be an R_1 and R_2 of $1e4$ and a C_1 and C_2 of $1.5e-11$.

Interpretation

One issue we encountered was with the model choosing Rs and Cs that were negative. We circumvented this by forcing the C-values to be positive, thus preventing the differential equations from working out correctly if the R-values are negative.

The model ends up basically eliminating the second filter entirely, so in future iterations, we would put more constraints on the Rs and Cs it could choose to prevent it from choosing Rs and Cs for the second filter that are effectively close to 0. This is due to the fact that we were unable to force the selected R's and C's to match the tau that we set.

In future iterations of the model, we might try to increase the realism of the model. For example, there is a standard set of capacitor values used in electrical engineering, so we might try to force the model to choose exclusively these capacitors and vary the resistor values more freely (rather than the other way around).


Abstract

What is the configuration of resistors and capacitors in a second order high pass filter that would result in a bode plot that aligns perfectly (or as close as possible) to the theoretical model for a high pass filter?

Our model settles upon resistors that are large enough to reduce the current enough for the bode to match. It also chooses a larger second resistor to further reduce the effect that current has on the bode plot.

For a high pass filter with a tau of $1.5\text{e-}5$, our model finds values as follows:

 - $R1 = 1.5\text{e}5$
- $R2 = 1.474\text{e}7$
- $C1 = 1.00\text{e-}10$
- $C2 = 1.02\text{e-}12$



Amplitude vs Frequency for the modelled circuitry.

The results that come out of our model make intuitive sense; however, it is very hard to determine whether the model has truly optimized the circuit or if it has just found resistor and capacitor values that work well. Either way our model is functional in that it will produce results that are valuable for designing and building a real second-order high pass filter.